

# Impulse Radar and CTBV Processing

Håkon A. Hjordland

Department of Informatics  
University of Oslo

Workshop on UWB implementations 2009-05-04

## Content

- 1 Radar
  - Basics
  - Swept threshold sampler
  - Stochastic resonance sampler
  - Implementation
- 2 CTBV signal processing
  - CTBV signal processing

# Content

- 1 Radar
  - Basics
    - Swept threshold sampler
    - Stochastic resonance sampler
    - Implementation
  
- 2 CTBV signal processing
  - CTBV signal processing

# A basic short range impulse radar

Main components:

- Pulse generator.
- Sampler with multiple-gigahertz sample rate.

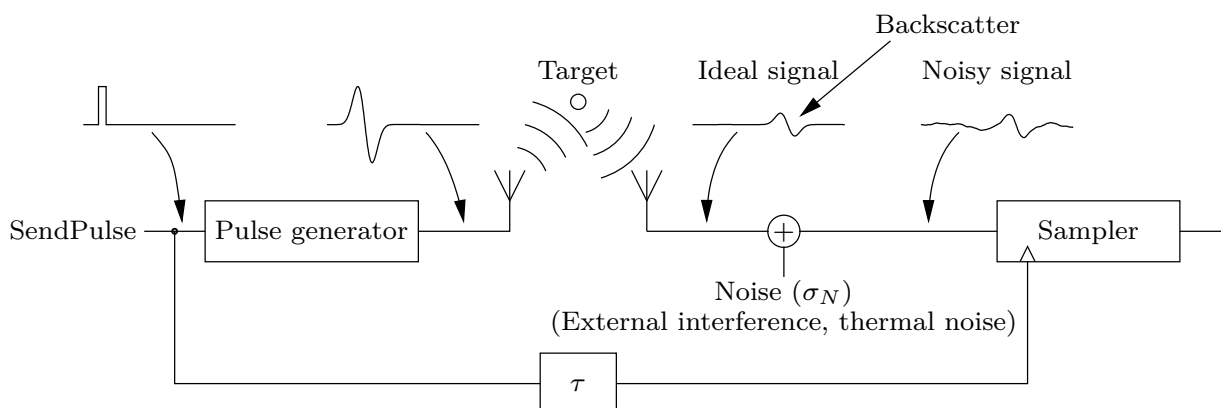


Figure: Basic radar.

# Content

- 1 Radar
  - Basics
  - Swept threshold sampler
  - Stochastic resonance sampler
  - Implementation
  
- 2 CTBV signal processing
  - CTBV signal processing

# Overview

Swept threshold sampler features:

- Novel approach.
- Exploits high speed digital performance of CMOS.
- Less analog signal processing.
- Simple circuits.
- Enables very high sample rate.

## How it works (1)

- Threshold input signal (analog  $\rightarrow$  continuous-time digital signal).
- Sample digital value at high rate.

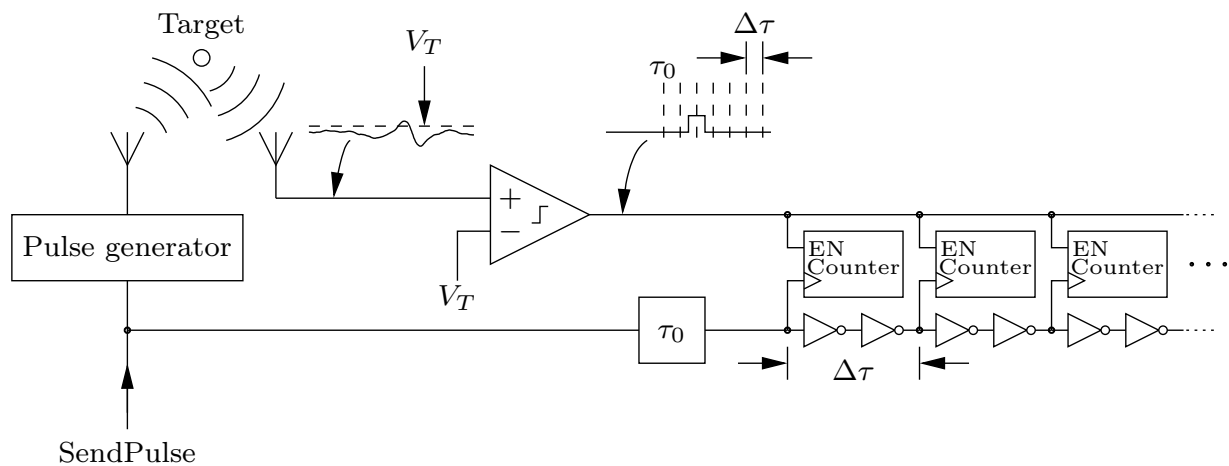


Figure: Swept threshold sampler.

## How it works (2)

- Repeat for all threshold levels.

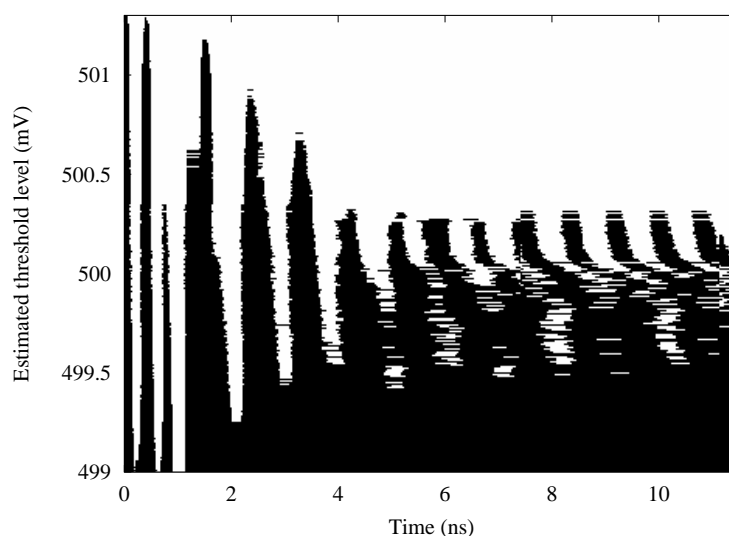


Figure: Sweep of threshold level.

## How it works (3)

- Sum vertically to get readout curve.
- Use repetition to average out noise.

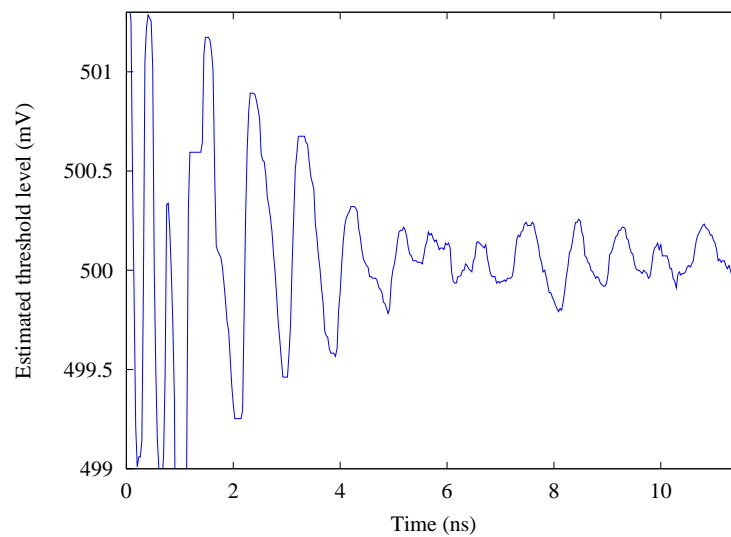


Figure: Radar readout curve.

## Content

- 1 Radar
  - Basics
  - Swept threshold sampler
  - **Stochastic resonance sampler**
  - Implementation
- 2 CTBV signal processing
  - CTBV signal processing

# What if there is very much noise?

If noise  $\approx$  signal:

- Leave threshold at DC level, don't sweep (the threshold will always be able to "get hold of" the signal due to the noise).
- Integrate a lot of samples.

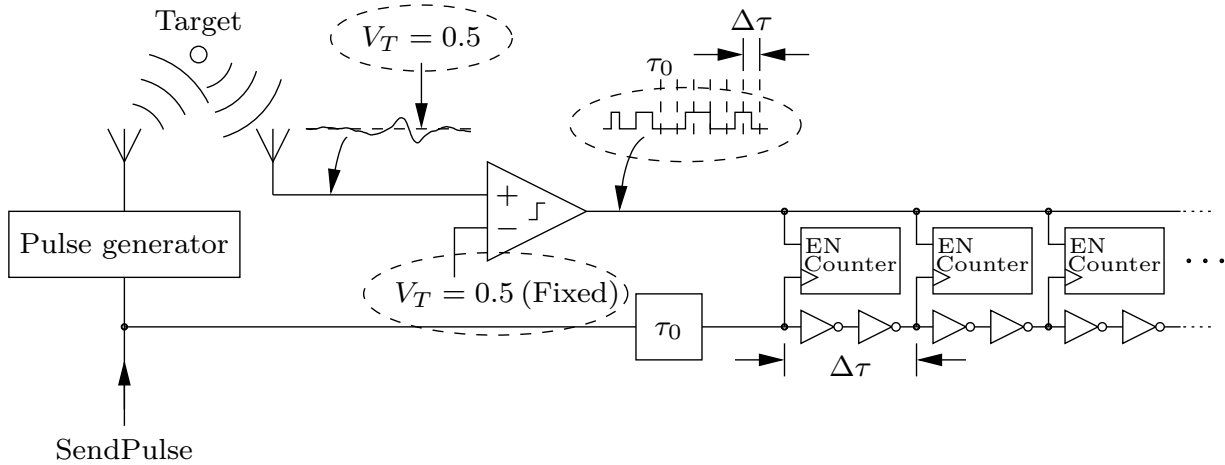


Figure: Stochastic resonance sampler.

# How to read out a signal

- Readout value is  $P(V_{in}(\tau) > 0.5)$  (plus some noise).
- Use that value to calculate signal value in units of  $\sigma_N$ .
- If  $\sigma_N$  is known, calculate the signal voltage value.

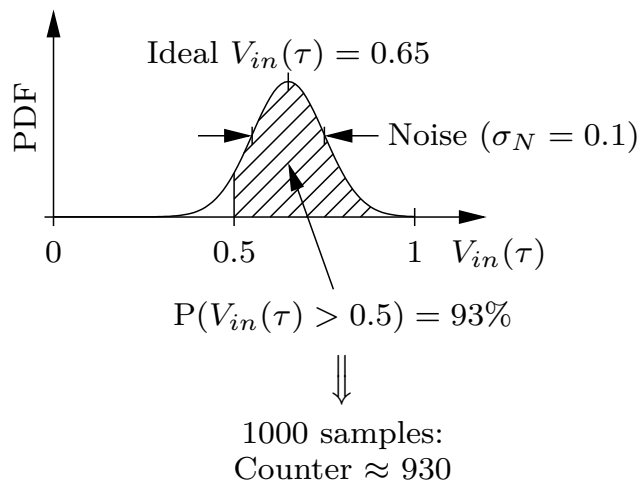


Figure: Stochastic resonance sampling principle.

# Properties of stochastic resonance sampler

- We call this “stochastic resonance sampling” (after the “stochastic resonance” effect).
- Simple system, but actually very close to ideal sampler.
- Requires very much noise (low SNR).
- Not currently used in the radar (too high SNR).

# Integration required to achieve a given SNR.

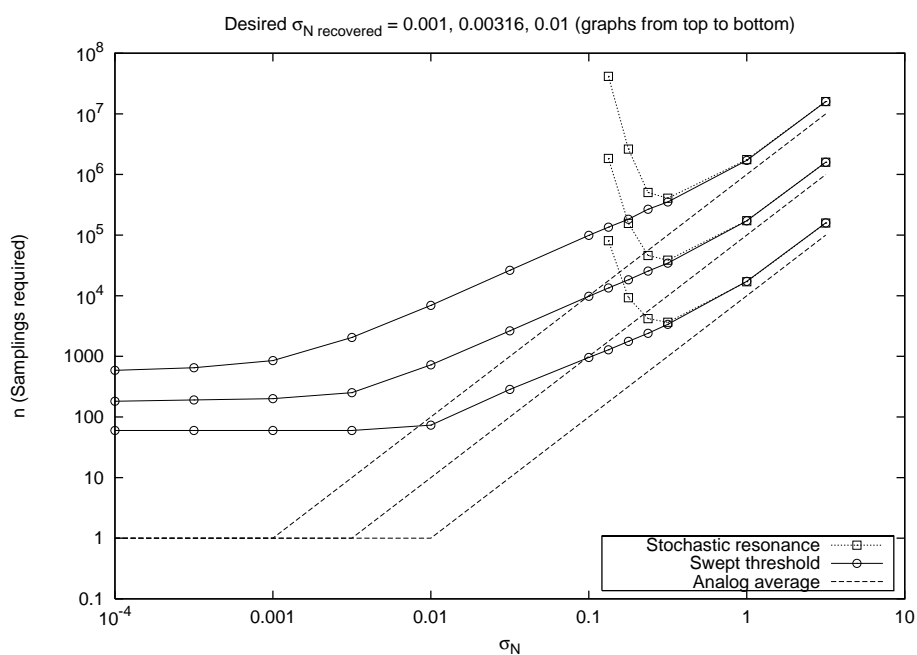


Figure: Integration required to achieve a given SNR.

# Content

- 1 Radar
  - Basics
  - Swept threshold sampler
  - Stochastic resonance sampler
  - Implementation
  
- 2 CTBV signal processing
  - CTBV signal processing

# Implementation

- Approx.  $1 \times 1$  mm 90 nm CMOS chip.
- Sweep controller logic on chip.
- SPI for setting registers and getting readout.
- 35 GHz sampling rate.
- 128 parallel samplers.
- 48 MHz PRF.
- Detecting millimeter-movement at close range.
- Detecting centimeter-movement at 15 m distance.



# Pulse generator.

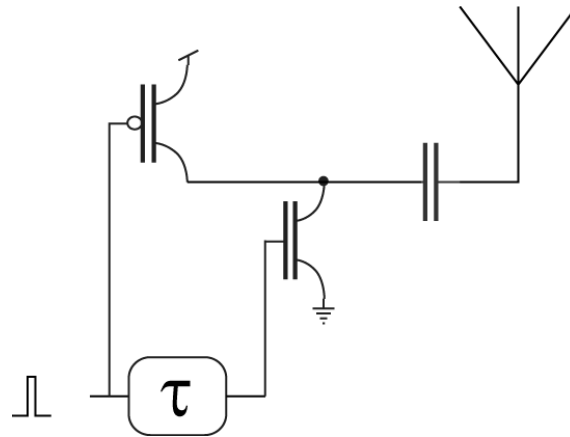


Figure: Pulse generator.

# Programmable initial delay.

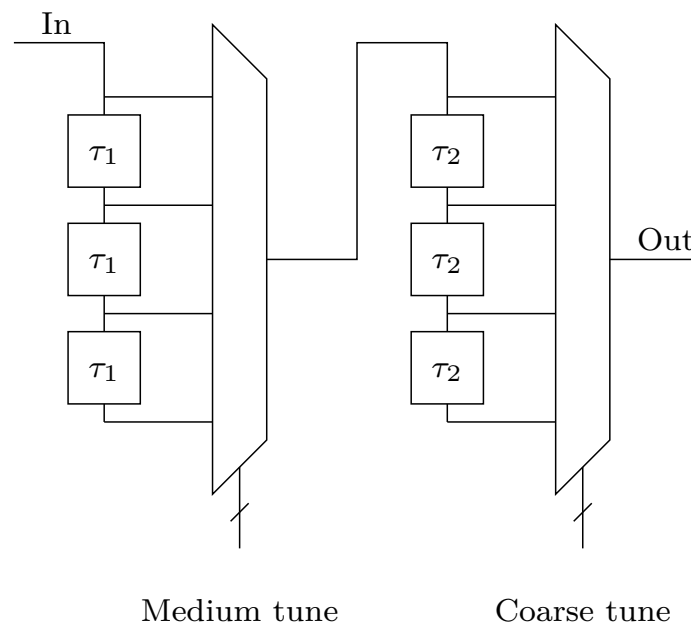


Figure: Programmable initial delay.

# Zoom-thresholder.

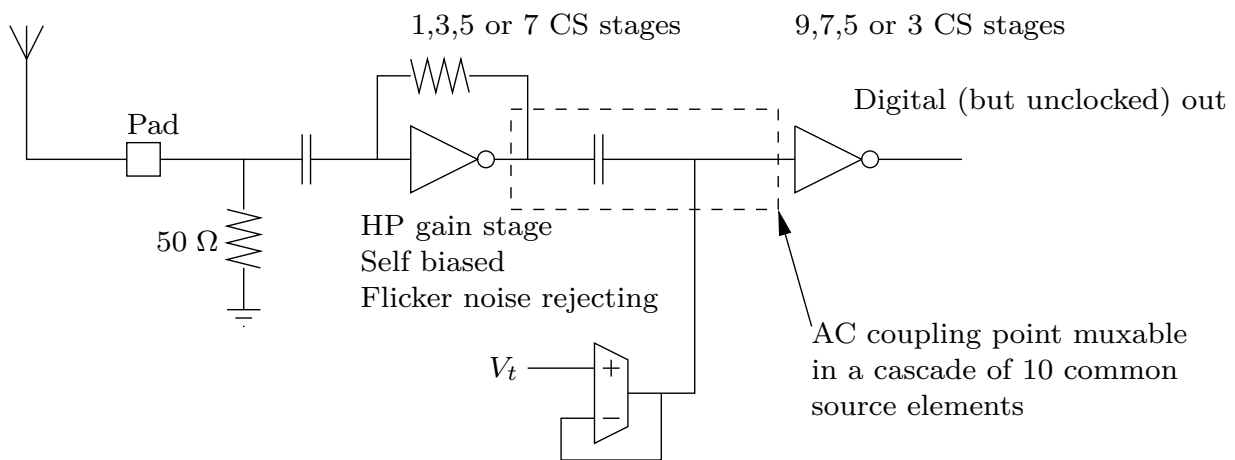


Figure: Zoom-thresholder.

# Zoom-thresholder common source element.

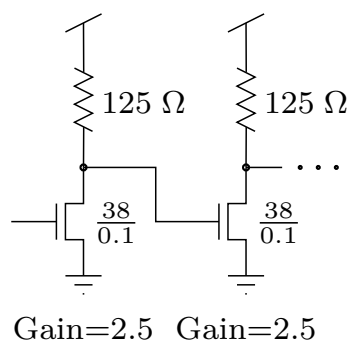


Figure: Zoom-thresholder common source element.

# Content

- 1 Radar
  - Basics
  - Swept threshold sampler
  - Stochastic resonance sampler
  - Implementation
  
- 2 CTBV signal processing
  - CTBV signal processing

# Continuous-Time Binary Value (CTBV) signal processing


Unlocked digital signals worked well for radar. Trying to generalize, introducing the term:  
 Continuous-Time Binary Value (CTBV) signal processing.

		<b>Time</b>	
		Discrete	Continuous
<b>Value</b>	Binary	Digital	CTBV
	Continuous	Analog sampled-data (switch-cap. . .)	Analog

Figure: Signal processing domains.

# CTBV signal representation.

Clocked digital signal:

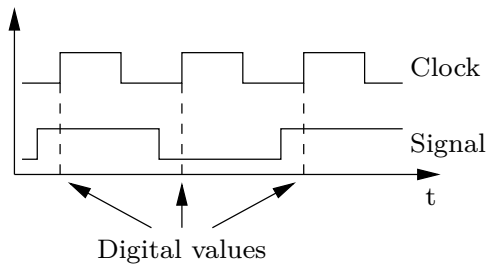

CTBV signal:



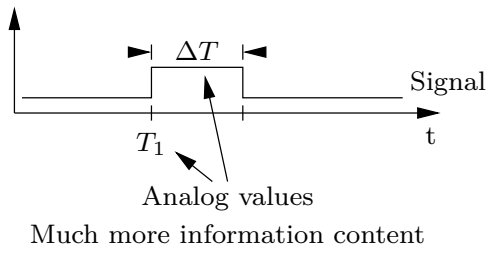


Figure: CTBV signal representation.


# CTBV example circuits.

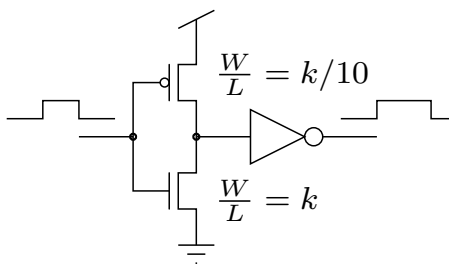

Pulse stretcher

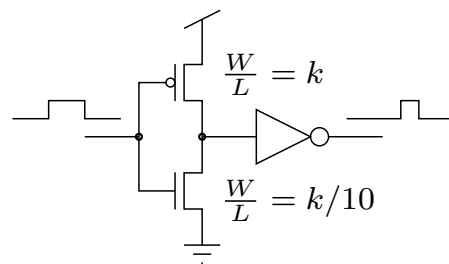

Pulse shortener

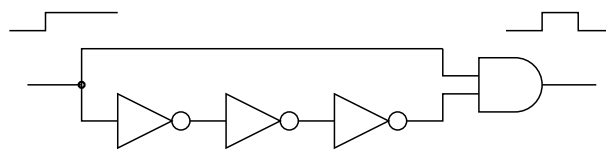

Edge to pulse

Figure: CTBV example circuits.

## CTBV operations

Some CTBV operations:

- Delay.
- Logic.
- Pulse shaping.
- Sampling.

## CTBV advantages

Advantages of CTBV signal processing:

- Advanced processing (pattern detection, etc.).
- Simple circuits.
- High speed. Gate delays (10–20 ps) or below (using time differences).
- No clock: Faster, saves power.
- Low power (simple, unlocked circuits).
- Perfect for fine-pitch CMOS technology (cheap, high speed digital, poor analog performance).

## CTBV challenges

Challenges with CTBV signal processing:

- Limited functionality: Not a general replacement for the other signal processing domains.
- Minimum pulse width requirements: Too short pulses might get lost.
- Phase noise: Limits the SNR of the signals (e.g. a pulse width).
- Device mismatch: Unpredictable delays.

## CTBV future work

What can be done with CTBV?

- Bubble-sorter (successfully implemented).
- Parallel counter (may be used in UWB-IR data receiver).
- More advanced circuits?

# The End

Questions?